

ECE 4623/5623
Homework #3 (Due: 10/17/2017)
Arithmetic Logic Unit (ALU)

1. Add an arithmetic logic unit (ALU) to your register transfer structure (HW #2).
2. The ALU should support the following 9 instructions.
 - (a) **Add:** add the values stored in two source registers and store the sum in a destination register.
 - (b) **Add Immediate:** add a value stored in a source register to a value provided through the switches and store the sum in a destination register.
 - (c) **Subtract:** subtract the values stored in two source registers and store the difference in a destination register.
 - (d) **Multiply:** multiply the values stored in two source registers and store the product in a destination register.
 - (e) **NAND:** compute a bitwise NAND between two source registers and store the logical result in a destination register.
 - (f) **AND:**
 - (g) **OR:**
 - (h) **Generate 8bit PseudoRandom Number:**
 - (i) **Create Your Own:**